

# Computer Organization & Architecture

“Computer Organization and Embedded Systems”

Carl Hamacher, Zvonko Vranesic, Safwat Zaky, Naraig  
Manjikian

# Control signals

- In each clock cycle:
  - Results of actions in one stage stored in inter-stage registers
  - Available for use by the next stage in the next clock cycle
- Data transferred from one stage to next in every clock cycle:
  - Inter-stage registers are always enabled
  - This is the case for registers RA, RB, RZ, RY, RM, and PC-Temp
- Contents of other registers, namely, PC, IR, and register file, must not be changed in every clock cycle
  - New data are loaded only when called for in a particular processing step
  - They must be enabled only at those times


# Control signals

- Role of multiplexers: select data to be operated on in any given stage
- Ex., in stage 3, MUXB:
- Selects immediate field in IR:
  - For instructions that use an immediate source operand
  - For instructions that use immediate data as offset when computing effective address of a memory operand
- Otherwise, it selects register RB


# Control signals

- Data selected by multiplexer MUXB are used by ALU
  - ALU is used only in step 3
    - Selection made by MuxB matters only during that step
  - To simplify required control circuit, same selection can be maintained in all execution steps
  - Similar observation can be made about MuxY


# Instruction Encoding

 

(a) Register-operand format

 

(b) Immediate-operand format

 


(c) Call format

# Control signals

- Assume register file has three 5-bit address inputs
  - Allows access to 32 general-purpose registers
- Addresses A and B determine registers to be read:
  - Connected to fields  $IR_{31-27}$  and  $IR_{26-22}$  in instruction register
- Address C selects the destination register:
  - Multiplexer MuxC selects the source of that address
  - Three-register instructions use bits  $IR_{21-17}$  and other instructions use  $IR_{26-22}$  to specify the destination register
  - Third input of multiplexer is address of the link register
  - New data are loaded into the selected register only when the control signal  $RF\_write$  is asserted
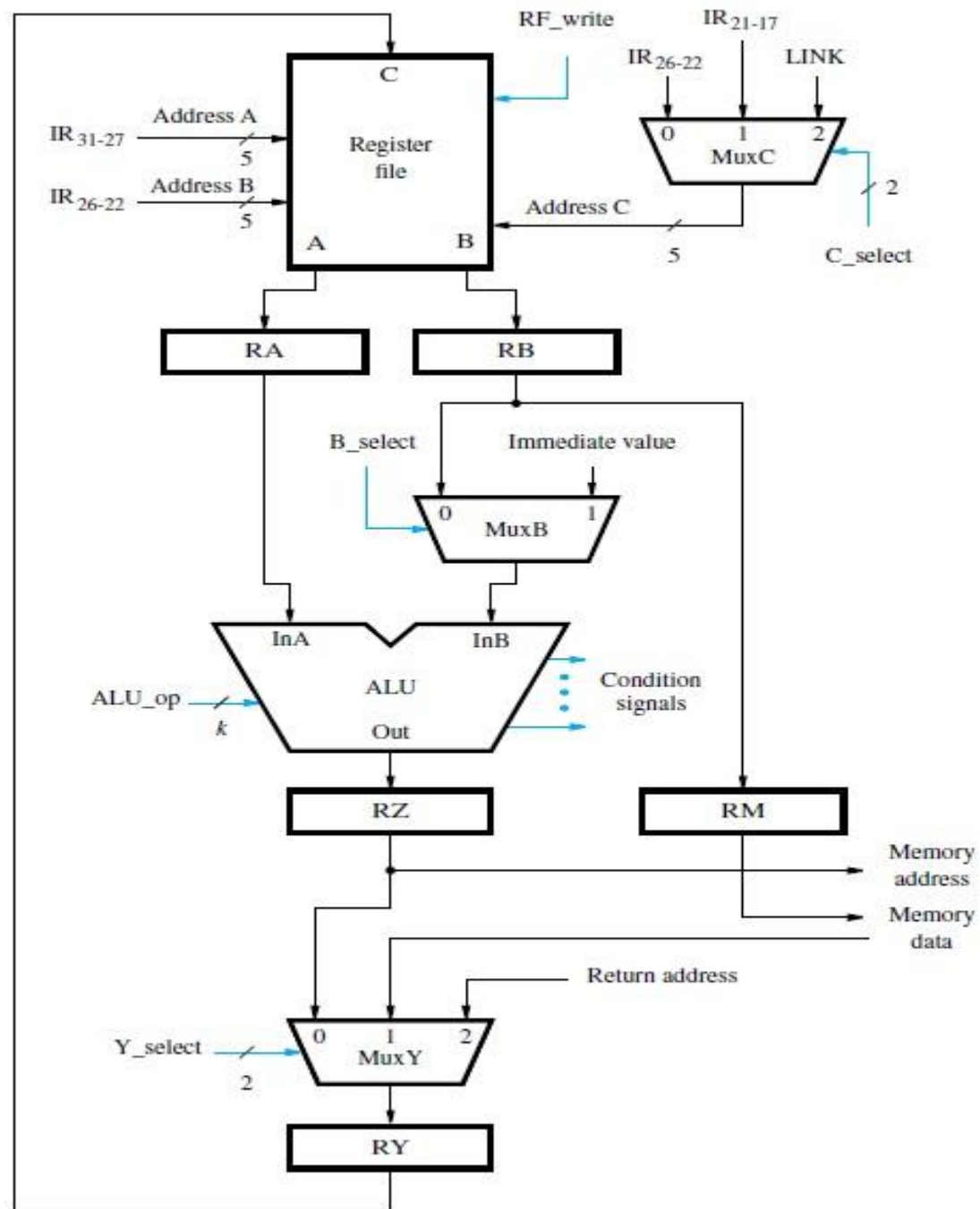
# Control signals

- Operation performed by ALU is determined by a k-bit control code, ALU\_op
  - Can specify up to  $2^k$  distinct operations
- When an instruction calls for two values to be compared
  - A comparator performs the comparison specified
  - Comparator generates condition signals that indicate result of the comparison
  - These signals are examined by control circuitry during the execution of conditional branch instructions to determine whether the branch condition is true or false.






# Control signals

- MuxMA must change selection in different execution steps
- Selects PC as source of memory address during step 1
  - When a new instruction is being fetched
- Selects register RZ during step 4 of Load and Store instructions
  - Contains effective address of memory operand

# Control signals

- Interface between the processor and the memory:
  - Two signals, MEM\_read and MEM\_write are used to initiate a memory Read or a memory Write operation.
  - When requested operation has been completed, interface asserts the MFC signal.
- Instruction register has a control signal, IR\_enable
  - Enables a new instruction to be loaded into the register.
  - During a fetch step, it must be activated only after MFC signal is asserted.

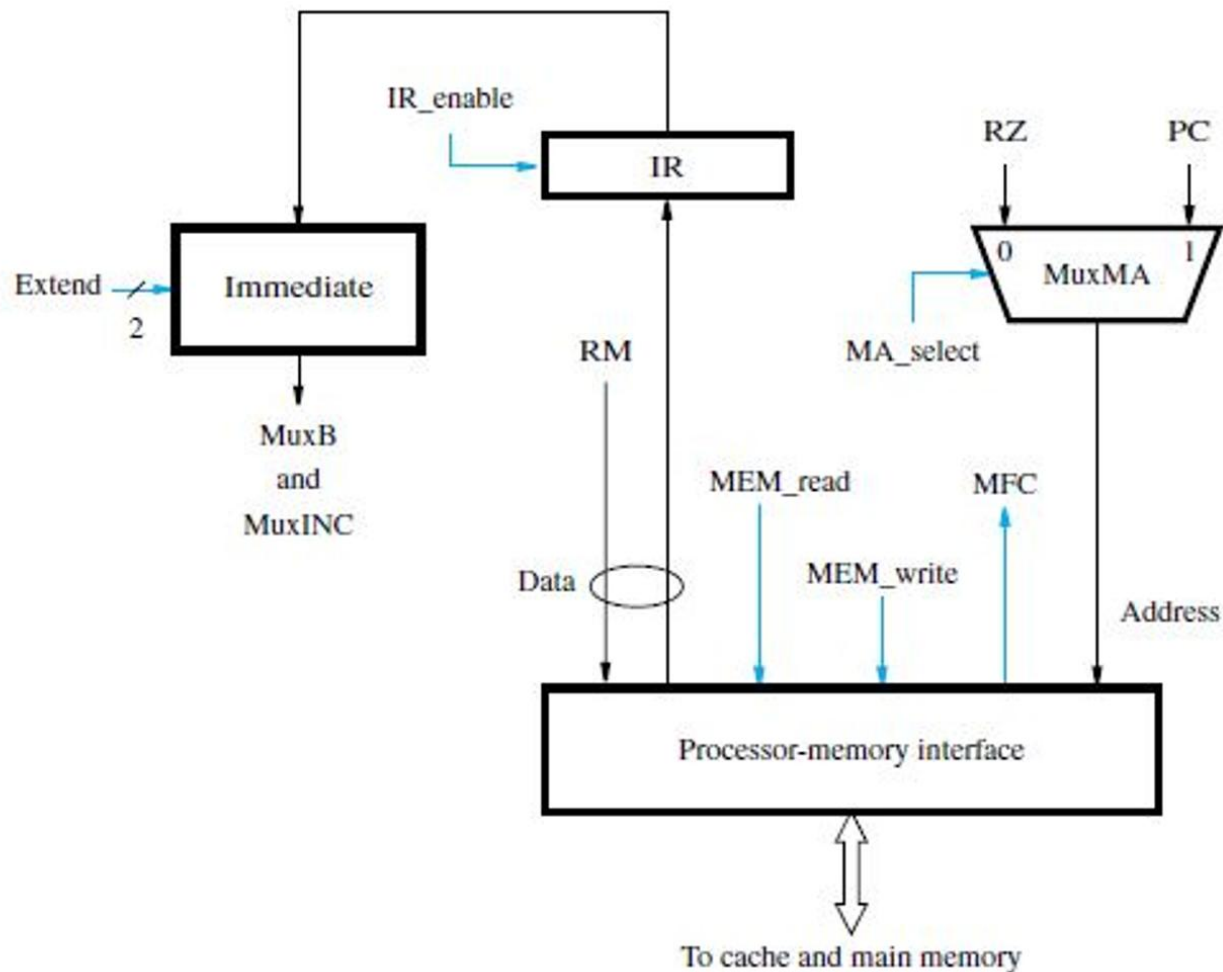
# Control signals: Processor-memory interface




# Control signals

- Signals that control the operation of the instruction address generator:
  - INC\_select signal selects the value to be added to the PC
  - Either constant 4 or branch offset specified in the instruction.
- PC\_select signal selects:
  - Either updated address
  - Or the contents of register RA
  - To be loaded into the PC when the PC\_enable control signal is activated

# Control signals: Address generator

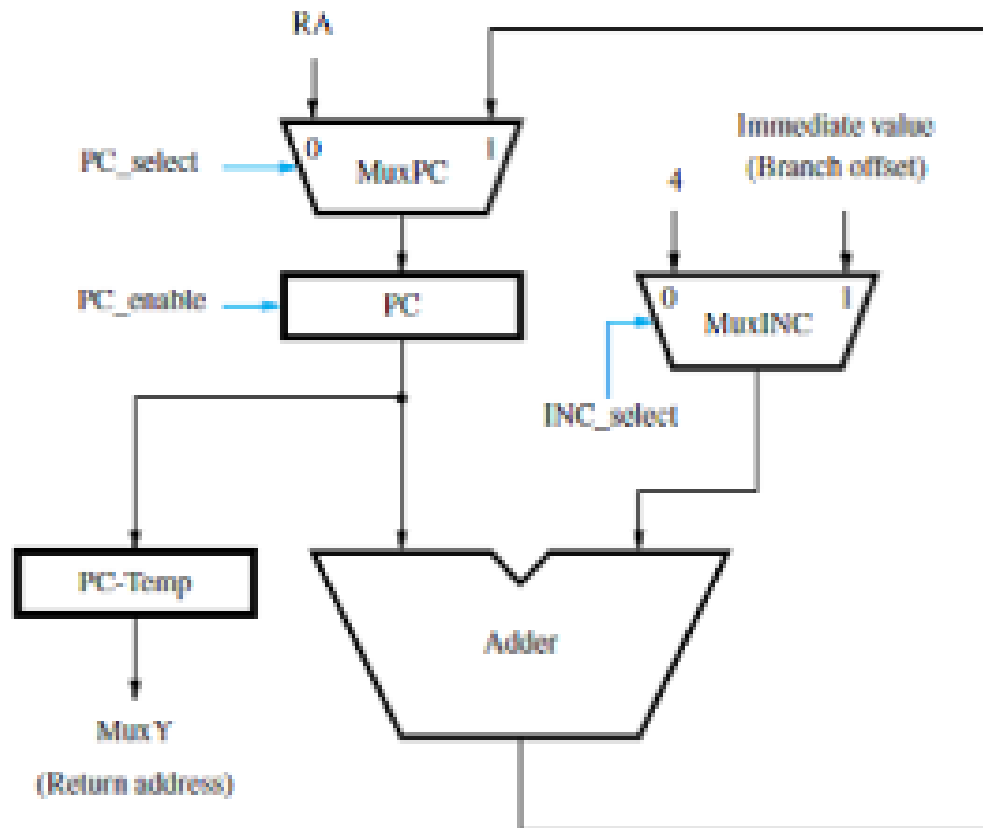
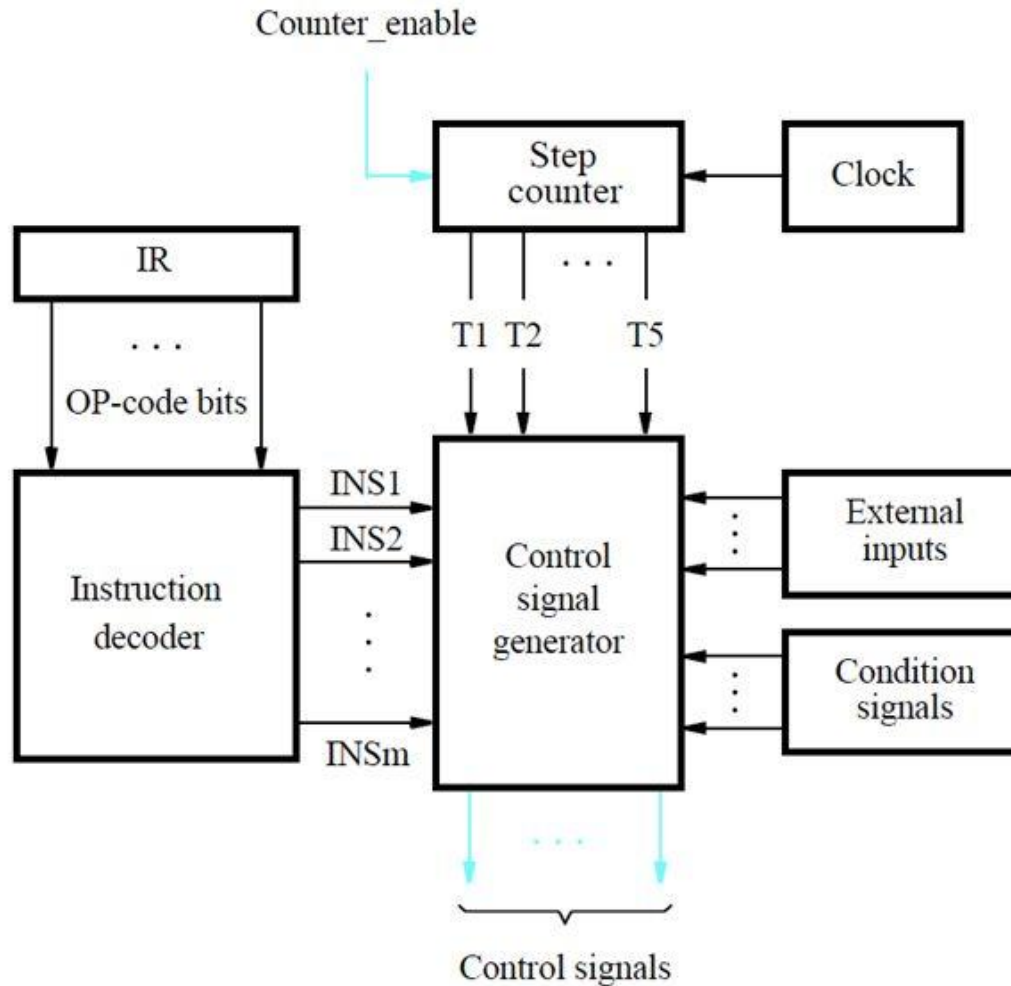
## Hardwired generation of control signals



**END**